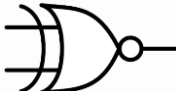


MCQ:




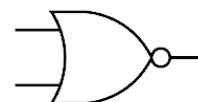
1. The circuit converting binary data in to decimal is
a) Encoder b) Multiplexer c) Decoder d) Code Converter
2. Which of the following logical operations is represented by the + sign in Boolean algebra?
a) Inversion b) AND c) OR d) complementation
3. Which logic gate represented by this symbol?
a) OR b) XNOR c) XOR d) NAND 
4. Total number of inputs in a half adder is _____.
a) 2 b) 3 c) 4 d) 1
5. The output of a NOR gate is HIGH if _____.
a) all inputs are HIGH b) any input is HIGH
c) any input is LOW d) all inputs are LOW
6. If A and B are the inputs of a half adder, the sum is given by _____.
a) A AND B b) A OR B c) A XOR B d) A EX-NOR B
7. If A, B and C are the inputs of a full adder then the sum is given by _____.
a) A AND B AND C b) A OR B AND C c) A XOR B XOR C d) A OR B OR C.
8. Half subtractor is used to perform subtraction of _____.
a) 2 bits b) 3 bits c) 4 bits d) 5 bits
9. The IC number of AND gate is
a) 7402 b) 7404 c) 7408 d) 7432
10. A register is defined as _____.
a) The group of latches for storing one bit of information
b) The group of latches for storing n-bit of information
c) The group of flip-flops suitable for storing one bit of information
d) The group of flip-flops suitable for storing binary information
11. The binary system use powers of.....for positional values.
a) 2 b) 10 c) 8 d) 16
12. The 2's complement of 1000_2 is _____
13. Flip flop is also called as _____.
a) Stable b) bistable c) Tri stable d) not stable
14. Which of the following expressions is not equivalent to x^1 ?
a) $x \text{ NAND } x$ b) $x \text{ NOR } x$ c) $x \text{ NAND } 1$ d) $x \text{ NOR } 1$

15. Which of the following is used as storage locations both in the ALU and the control section of a computer?

- a) Accumulator b) Register c) Adder d) Decoder

16. Which logic gate is represented by this truth table?

INPUT A	INPUT B	OUTPUT
0	0	0
1	0	0
0	1	0
1	1	1

- a)  b) 
c)  d) 

17. What is the function of a NOT gate?

- a) Inverts its input b) Outputs 1 if both inputs are 1
c) Prevents errors d) Outputs 0 if both inputs are 0

18. What is the output Z of this logic circuit if A = 1 and B = 1

- a) 0 b) 1



19. The truth table for an S-R flip-flop has how many VALID entries?

- a) 1 b) 2 c) 3 d) 4

20. The flip-flops which has not any invalid states are _____

- a) S-R, J-K, D b) S-R, J-K, T c) J-K, D, S-R d) J-K, D, T

21. What does the circle on the clock input of a J-K flip-flop mean?

- a) Level enabled b) Positive edge triggered c) negative edge triggered d) Level triggered

22. What is the binary equivalent of hexadecimal A5?

- a) 10101101 b) 10100101 c) 11010011 d) 10101010

23. What is the decimal equivalent of octal 20?

- a) 16 b) 18 c) 22 d) 20

24. What is the decimal equivalent of hexadecimal B4?

- a) 180 b) 170 c) 160 d) 150

25. Sequential circuit contains


- a) No memory element b) Atleast one memory element

- c) All inputs applied simultaneously d) None of the above
26. The output of a logic gate is 1 when all its inputs are at logic 0, the gate is either
a) AND, XNOR b) NAND, XNOR c) NOR, XNOR d) OR, XOR
27. The circuit converting binary data in to decimal is
a) Encoder b) Multiplexer
c) Decoder d) Code Converter
28. The flip-flops which has not any invalid states are _____
a) S-R, J-K, D b) S-R, J-K, T
c) J-K, D, S-R d) J-K, D, T
29. What is the octal equivalent of decimal 30?
a) 36 b) 38 c) 37 d) 35
30. Sequential circuit contains
a) No memory element b) Atleast one memory element
c) All inputs applied simultaneously d) None of the above
31. Let * be defined as a Boolean operation given as $x * y = x^1y^1 + xy$ and let $C = A * B$.
If $C = 1$ then
a) $A = B$ b) $A = B'$ c) $C \cdot A + B = 1$ d) None of the above
32. The operation which is commutative but not associative is
a) AND b) OR c) EXOR d) NAND
33. A flip-flop is a binary cell capable of storing one-bit information
a) True b) False
34. Combinational circuit will have memory
a) True b) False
35. Determine the values of A, B, C, and D that make the sum term $A^1 + B + C^1 + D$ equal to zero?
Two bits can be compared using
a) AND b) OR c) EXOR d) EXNOR
36. What does the circle on the clock input of a J-K flip-flop mean?
a) Level enabled b) Positive edge triggered
c) negative edge triggered d) Level triggered
37. What is the function of a NOT gate?
a) Inverts its input b) Outputs 1 if both inputs are 1
c) Prevents errors d) Outputs 0 if both inputs are 0
38. What gate is this table for?

A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

- a) AND b) OR c) NOT d) XOR

39. What logic gate is this?

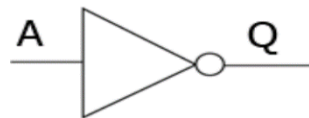

- a) AND b) OR c) NOT d) XOR

40. Which of the following is used as storage locations both in the ALU and the control section of a computer?

- a) Accumulator b) Register c) Adder d) Decoder


41. A logic state can only be....

- a) On or 1 b) Off or 1 c) 1 or 0 d) In and out

42. Which of the following expressions is not equivalent to x^1 ?

- a) $x \text{ NAND } x$ b) $x \text{ NOR } x$ c) $x \text{ NAND } 1$ d) $x \text{ NOR } 1$

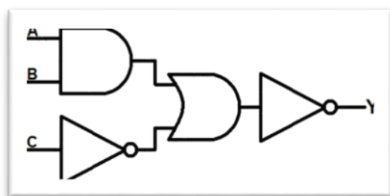43. In a multiplexer the selection of a particular input line is controlled by a set of _____ lines.



44. What is the output Y of this logic circuit if $A = 1$, $B = 1$, and $C = 1$?

- a) 0 b) 1
45. Which of the following is not a Boolean operation?
b) NOT b) AND c) BUT d) XOR

46. What is the decimal equivalent of octal 30?
 a) 36 b) 24 c) 37 d) 35
47. The binary system use powers of.....for positional values.
 a) 2 b) 10 c) 8 d) 16
48. The truth table for an S-R flip-flop has how many VALID entries?
 a) 1 b) 2 c) 3 d) 4
49. What is the binary equivalent of hexadecimal A5?
 a) 10101101 b) 10100101 c) 11010011 d) 10101010
50. What is the octal equivalent of binary 1101?
 a) 13 b) 14 c) 15 d) 16
51. How is a J-K flip flop made to toggle?
 a) J=0, K=0 b) J=1, K=0 c) J=0, K=1 d) J=1, K=1
52. The IC number of NOT gate is
 a) 7402 b) 7404 c) 7408 d) 7432
53. Which of the following gate is a universal gate?
 a) AND b) XOR c) NOT d) NAND
54. What is the decimal equivalent of octal 30?
 a) 36 b) 24 c) 37 d) 35
55. A Binary Digit is called a
 a) Byte b) Bit c) Nibble d) None of above
56. Let * be defined as a Boolean operation given as $x * y = x^1 y^1 + xy$ and let $C = A * B$.
 If $C = 1$ then
 a) $A = B$ b) $A = B'$ c) $A + B = 1$ d) None of the above
57. The operation which is commutative but not associative is
 a) AND b) OR c) EXOR d) NAND
58. A flip-flop is a binary cell capable of storing one-bit information
 a) True b) False
59. Combinational circuit will have memory
 a) True b) False
60. Determine the values of A, B, C, and D that make the sum term $A^1 + B + C^1 + D$ equal to zero?
 Two bits can be compared using
 a) AND b) OR c) EXOR d) EXNOR
61. What does the circle on the clock input of a J-K flip-flop mean?
 a) Level enabled b) Positive edge triggered

- c) negative edge triggered d) Level triggered

62. What is the function of a NOT gate?


- a) Inverts its input b) Outputs 1 if both inputs are 1
c) Prevents errors d) Outputs 0 if both inputs are 0

63. What gate is this table for?

A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

- b) AND b) OR c) NOT d) XOR

64. What logic gate is this?

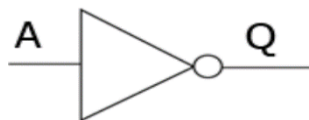

- a) AND b) OR c) NOT d) XOR

65. Which of the following is used as storage locations both in the ALU and the control section of a computer?

- a) Accumulator b) Register c) Adder d) Decoder

66. A logic state can only be....

- b) On or 1 b) Off or 1 c) 1 or 0 d) In and out


67. Which of the following expressions is not equivalent to x^1 ?

- b) $x \text{ NAND } x$ b) $x \text{ NOR } x$ c) $x \text{ NAND } 1$ d) $x \text{ NOR } 1$

68. In a multiplexer the selection of a particular input line is controlled by a set of _____ lines.

69. Choose all the Boolean logic gates

- a) NOT b) AND
c) BUT d) XOR

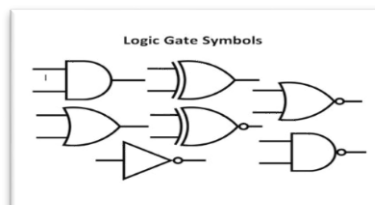

70. What is the octal equivalent of decimal 30?

- b) 36 b) 38 c) 37 d) 35

71. The binary system use powers of.....for positional values.

- a) 2 b) 10 c) 8 d) 16

72. The truth table for an S-R flip-flop has how many VALID entries?

- a) 1 b) 2 c) 3 d) 4

73. What is the binary equivalent of hexadecimal A5?

- a) 10101101 b) 10100101 c) 11010011 d) 10101010

74. What is the octal equivalent of binary 1101?

- b) 13 b) 14 c) 15 d) 16

75. The output of a NOR gate is HIGH if

- a) all inputs are HIGH b) any input is HIGH
c) any input is LOW d) all inputs are LOW